



Figure 2.10 Illustration of the pin connections on three commercially available integrated circuits that implement logic gates. Pins 7 and 14 supply power (zero volts and five volts) to run the circuit.