



**Figure 2.11** Illustration of how one type of flip-flop reacts to a sequence of inputs. The flip-flop output changes when the input transitions from 0 to 1 (i.e., from zero volts to five volts).