



**Figure 2.13** Illustration of (a) a binary counter, and (b) a sequence of input values and the corresponding outputs. The column labeled *decimal* gives the decimal equivalent of the outputs.