



Figure 2.15 An illustration of how a clock can be used to create a circuit that performs a sequence of six steps. Output lines from the counter connect directly to input lines of the demultiplexer.