



Figure 2.7 Illustration of gate interconnection. The output from one logic gate can connect directly to the inputs of other gates.